



AN2067 APPLICATION NOTE

VIpower: DIMMABLE WHITE LEDS POWER SUPPLY WITH VIPer53

In the same way that LED manufacturers succeed to realize blue LEDs, they now propose white LEDs inside a monolithic chip, or so called "single-chip white" LEDs.

A current source is the more appropriate way to drive LEDs. For a maximum of flexibility, a large voltage range must be supported at the output due to the large threshold of these white LEDs, and the possible serial arrangement of them.

Furthermore, if these LEDs have to be dimmable, they must be driven with a PWM (current generator).

As a consequence, key features for this off-line power supply is a current generator, which can work as a Pulses Width Modulated mode, with a wide output voltage range, and must also suite any input voltage standard, and a galvanic isolation.

1. VIPer53 DESCRIPTION

VIPer53, the first multichip device of the VIPer family has been chosen to fulfill the requirements. It features very low R_{dson} of 1Ω allowing to deliver a typical power of 35W in wide range in a standard DIP-8 package without a heatsink, answering the

need for higher efficiency and reduced space thanks to a lower power dissipation.

1.1. General features


The block diagram is given on Figure 1. An adjustable oscillator is driving a current controlled PWM at a fixed switching frequency. The peak drain current is set for each cycle by the voltage present on the COMP pin. The useful range of the COMP pin extends from 0.5V to 4.5V, with a corresponding drain current range from 0A to 2A. This COMP pin can be either used as an input when working in secondary feedback configuration, or as an output when the internal error amplifier connected on the VDD pin is operating in primary feedback to regulate the VDD voltage to 15V.

The VDD under voltage comparator drives a high voltage startup current source, which is switched off during the normal operation of the device. This feature together with the burst mode capability allows to reach very low level of input power in standby mode, when the converter is lightly loaded.

Table 1. White LEDs Power Supply Specification

Parameter	Name	Conditions	Min	Typ	Max	Unit
Output current	I_{OUT}	$V_{OUT} = 20V$	200		1000	mA
Output voltage	V_{OUT}	$I_{OUT} = 1A$	5		40	V
Output Power	P_{OUT}				40	W
Input Voltage	V_{IN}		82		265	V_{AC}

Figure 1. VIPer 53 block diagram

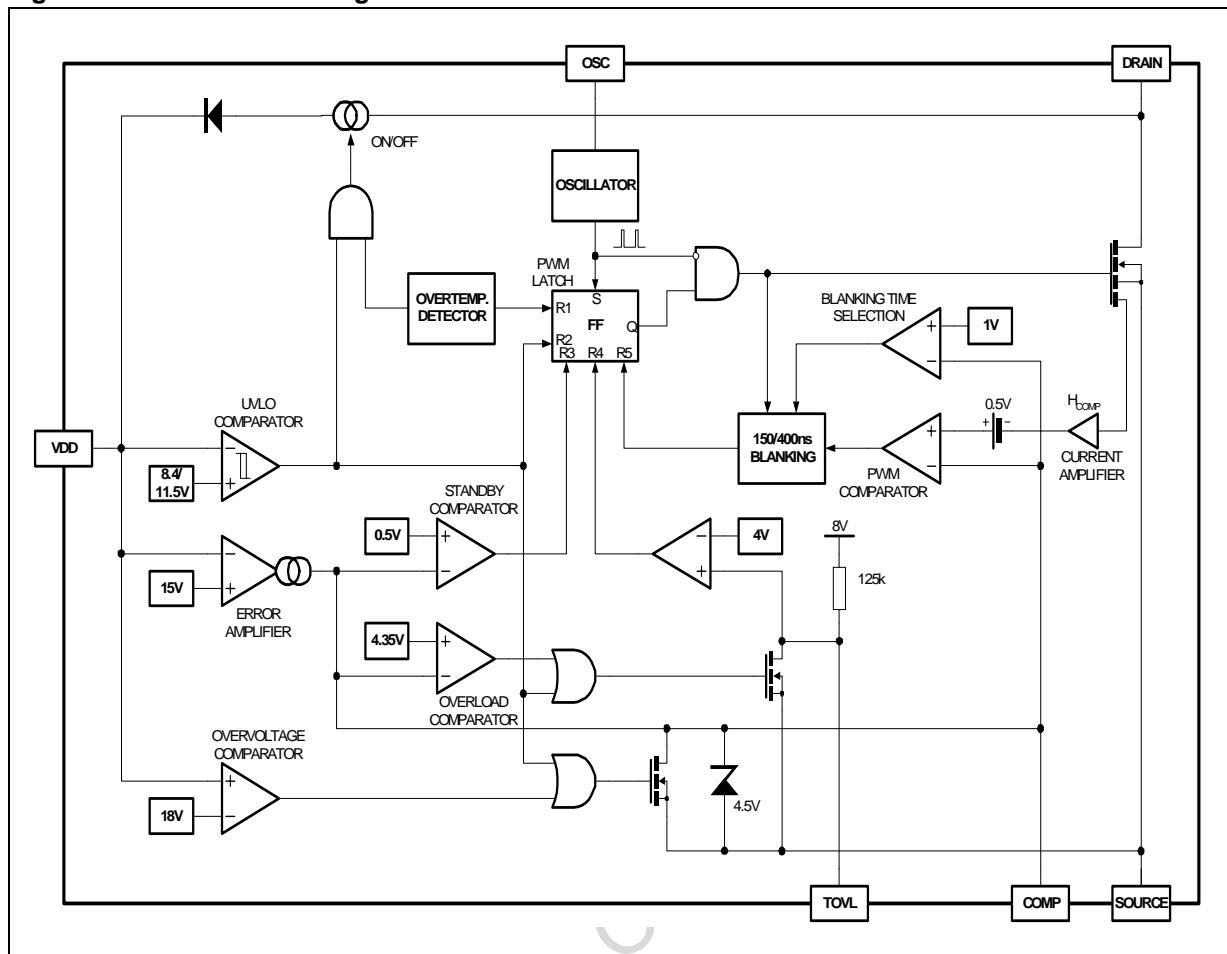

1.2. Overload protection

A threshold of 4.35V typical has been implemented on the COMP pin. This overload threshold is 150mV below the clamping voltage of 4.5V which corresponds to the current limitation of the device. In case of a COMP voltage exceeding the overload threshold, the pull up resistor on the TOVL pin is released and the external capacitor connected on this pin begins to charge. When reaching a value of 4V typical, the device stops switching and remains in this state until the VDD voltage reaches V_{DDoff} , or resumes normal operation if the COMP voltage returns to a value below the overload threshold.

The drain current that the device is able to deliver without triggering the overload threshold is called “current capability”, specified as I_{Dmax} in the data sheet. This value must be used to size correctly the converter versus its maximum output power. When an overload occurs on secondary side of the

converter, the output power is first limited by the current limitation of the device. If this overload is lasting for more than a time constant defined by a capacitor connected on the TOVL pin, the device is reset, and a new restarting sequence is initiated by turning on the startup current source. The capacitors on the VDD pin and on the TOVL pin will be defined together in order to insure a correct startup and a low restart duty cycle in overload or short circuit operation. Here are the typical corresponding formulas:

$$C_{OVL} > 12.5 \times 10^{-6} \cdot t_{ss}$$

$$C_{VDD} > 8 \times 10^4 \cdot \left(\frac{1}{D_{RST}} - 1 \right) \cdot \frac{C_{OVL} \cdot I_{DDch2}}{V_{DDhyst}}$$

$$C_{VDD} > \left(\frac{I_{DD1} \cdot t_{ss}}{V_{DDhyst}} \right)$$

Where t_{ss} and D_{RST} are respectively the time needed for the output voltages to pass from 0V to

their nominal values at startup, and the restart duty cycle in overload or short circuit condition. A typical value of 10 % is generally set for this last parameter, as it insures that the output diodes and the transformer don't overheat. The other parameters can be found in the data sheet of the device.

As the VDD capacitor has to respect two conditions, the maximum value will be retained to define its value.

1.3. Stand-by operation

On the opposite load configuration, the converter is lightly loaded and the COMP voltage is decreasing until reaching the shutdown threshold at typically 0.5V. At this point, the switching is disabled and no more energy is passed on secondary side. So, the output voltage is decreasing and the regulation loop is rising again above the shutdown threshold, thus resuming the normal switching operation. A burst mode with pulse skipping is taking place, as long as the output power is below the one corresponding to the minimum turn on of the device. As the COMP voltage is working around 0.5V, the peak drain current is very low (it is actually defined by the minimum turn on time of the device, and by the primary winding of the transformer) *and no audible noise is generated*.

In addition, the minimum turn on time depends on the COMP voltage. Below 1V (V_{COMPbl}), the blanking time increases to 400ns, whereas it is 150ns for higher voltages. The minimum turn on time resulting from these values are respectively 600ns and 350ns, when taking into account the internal propagation time. This feature brings the following benefit:

- This brutal change induces an hysteresis between normal operation and burst mode which is reached sooner when the output power is decreased.
- A short value in normal operation insures a good drain current control in case of short circuit on secondary side.
- A long value in standby operation reinforces the burst mode by skipping more switching cycles, thus decreasing switching losses.

More details regarding the standby operation can be found in the data sheet. See also the practical

results obtained in the corresponding section of this document.

2. WHITE LEDS POWER SUPPLY

2.1. Schematic

The power topology is an off-line fly-back, working at a fixed frequency of 66KHz.

The overall schematic is presented on Figure 2.

2.1.1. Primary section

On the left hand side of the schematic, there is the fuse F1, inrush current limiter CTN1, input filter T1, followed by the rectifier BR1 and its bulk capacitance C3.

R4, C4 and D4 built the RCD clamped, for discharging the leakage inductance of the transformer.

D2, R2 and C5 is the rectifier and filtering of the primary auxiliary winding, used in forward mode (refer to Section 3). This generates a voltage supply from 21 V up to 80 V, proportional to turns ratio between main primary winding and auxiliary primary winding, and versus input voltage range (110 V_{AC} up to 250 V_{AC}).

A serial voltage regulator is required to supply the VIPer 53 with the correct voltage (around 12 V). It is built with R14, DZ14, Q1 and C12. Notice that the V_{CE0} of this transistor must be higher than 80 V. This transistor may also dissipate 0.7 W when input voltage is 250 V_{AC}.

The COMP pin filter is done using C8, R9 and C9.


2.1.2. Transformer

By definition, a current generator may have a large output voltage variation, according to the output load.

Then, if auxiliary winding is used in fly-back mode, there could be a large voltage variation on auxiliary winding as it is proportional to the reflected voltage. So, it will be used in forward mode in order to limit the voltage variation for supplying the VIPer53.

In order to guaranty the functionality even with low output voltage load, an auxiliary winding at secondary side has been added, instead using the main secondary output to supply the regulation loop and the voltage limitation (using the TSM 101). For similar reasons, this auxiliary winding will be also used in forward mode.

Figure 2. Current Generator Schematic

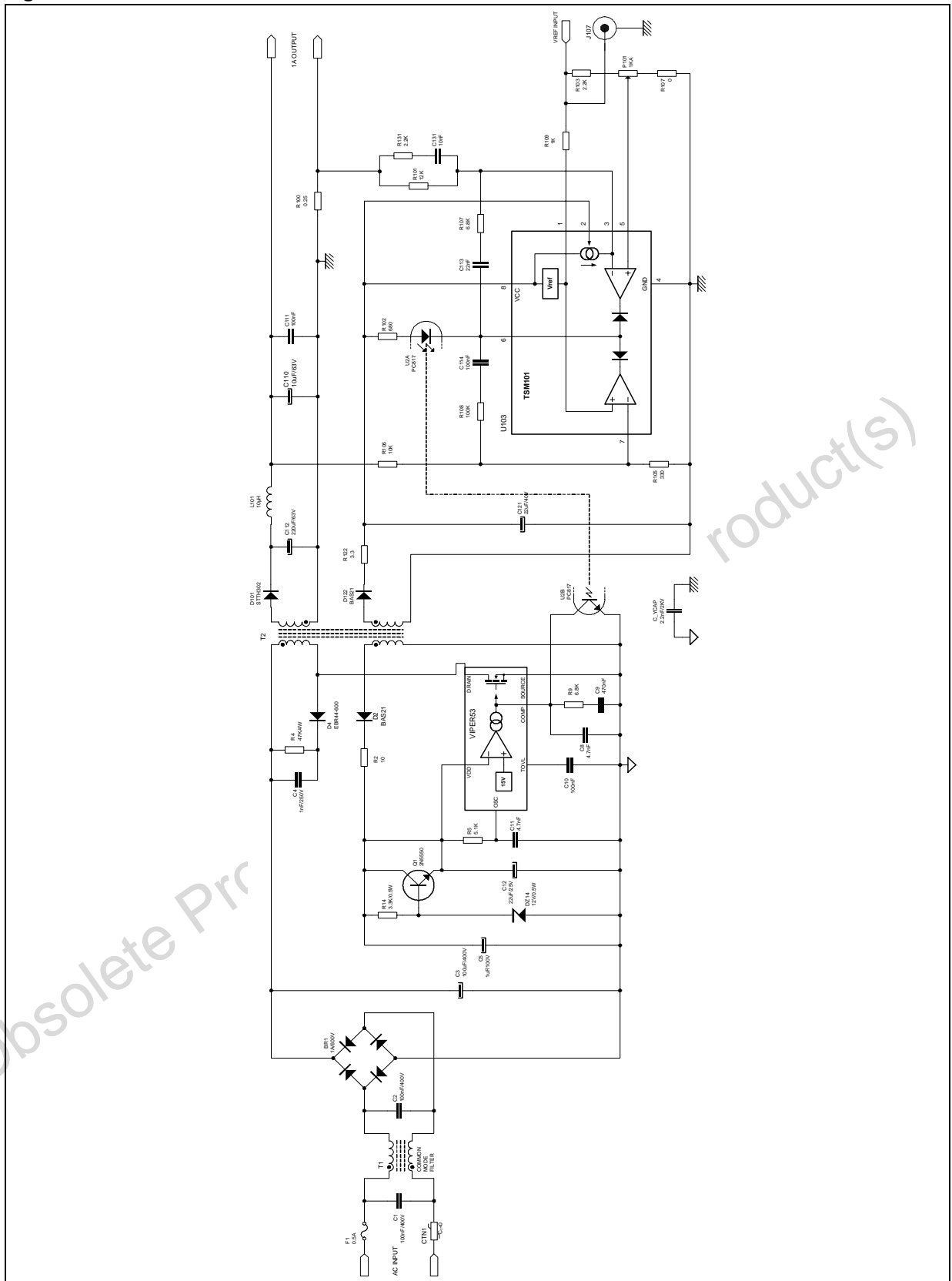

2.1.3. Secondary section

On the right hand side of the schematic, the secondary winding is used in fly-back mode. D101, C112 are respectively the rectifying diode and its filtering. L101 and C110 build another low pass filter.

The auxiliary secondary winding used in forward mode (refer to Section 3) in association with R122, D122 and C121 built the rectifier and filtering for the supply of the regulation loop, using a dedicated component (TSM101). This supply is independent from the load voltage.

TSM 101 has been design for voltage and current controller, which can be used for the control of a current generator, in association with a voltage limitation. It includes its own reference voltage (bandgap), and two operational amplifiers.

2.1.4. Current regulation loop

The output current is sensed through the shunt resistor R100. The shunt voltage is amplified using R101 and R107 in association with one OPamp of the TSM 101, building the error amplifier. The current target is set through the trimmer P101. R103 and P101 provide a fraction of the reference voltage provided by the TSM 101 (U103).

There is also another way to set the current target, using the connector J107 for dimming (see Section 2.2).

C113 with R107 is the integrator network of this amplifier, in order to cancel the static error of the regulation loop.

Then, the regulation loop continue with the optocoupler U2 (diode and transistor). This set the level of the COMP pin filter, which set the peak drain current VIPer53's power cell (current control mode). Thus, the energy stored inside the transformer during each cycles is transferred on the secondary side, which supply the output current.

R131 and C131 is a phase lead network in order to compensate the phase delay due to L101/C110 filter, for whole loop stability purpose.

2.2. Dimming

2.2.1. Dimming purpose

The main purpose of this application is to supply "single-chip white LEDs", and to dim the brightness of these LEDs.

Because the white color is obtained from two peaks in the spectrum (a blue ray and a yellow ray), there is a dependency between the driving current and the white color spectrum.

2.2.2. Dimming in the application

This application do not propose any PWM and its oscillator circuitry, which can be easily found in dedicated literature. The way to proceed is to apply an external PWM signal on the node VREF_INPUT.

Provided that output impedance of the generator is not higher than 50 Ω , the input voltage is forced by the external generator instead of the DC reference voltage of the TSM 101.

The low level voltage of this PWM signal must be 0V, and high level voltage must be around 1 V.

Then, the peak current of the PWM generator can be set using the trimmer P101, as in DC mode, from 0 up to 1 A.

The maximum frequency allowed is limited by dynamic behavior of the PWM current generator (refer to Section 2.2.4). The best way to use this power supply, is to set the lowest frequency convenient for human eye versus flicker. The highest the period, the highest the dimming range.

2.2.3. Audible noise

When using the power supply with a PWM signal, some audible noise may be heard, especially if the frequency of the external signal is inside the audible range.

This noise is emitted by the core of the transformer, and is a normal way to work. This noise is proportional to the output power transferred through it.

This noise can be reduced by optimization of the transformer.

2.2.4. Dynamic behavior of the current regulation loop

As explain above, the power supply must be able to generates a PWM current, at a sufficient frequency in order to avoid flicker, with the possibility to adjust the duty cycle. The shortest the time response of the regulation loop, the more linear will be the 0 % up to 100 % characteristics of the dimming range.

Thanks to the threshold of LED, it is possible to pulse its current instead to pulse its voltage. Then, the voltage can be maintained, it avoid to charge and discharged the output capacitances. This helps a lot for dynamic behavior of the current generator, since the output filtering capacitance are quite large.

The dynamic behavior of this current generator is limited by several root causes in the whole schematic.

First origin of limitation is the RC couple R101 + R107 / C113. When the reference level is changing on the error amplifier (TSM 101-pin 5), the OPamp must move to this new operating point, by charging the node TSM 101-pin 3. This is limited by the charging of the capacitor C113 through the resistor R101 + R107.

Secondly, the filtering capacitance C121 must be large enough in order to properly sustain the supply voltage of the OPamp and the resistor R102. Effectively, during a transient, the OPamp has to compensate its output level for loop stabilization. Then, the dynamic behavior is limited by the (dis)charging of the capacitor C113 through the resistor R102, once the supply voltage of the amplifier is stable during that transient.

Third, the serial resistance of the load, plus the shunt resistance R100, and the serial resistor of the capacitor C112 are limiting the time response of the current generator. When switching the output current from OFF (low current level) to ON (high current level), the output voltage has to increase of:

$$\Delta V_{out} = \Delta I_{out} \cdot (R_{sload} + R_{shunt})$$

But, the output current capability will be limited for a while, until the charging of the capacitance C112 is not completed. When this capacitor is charged, then the current capability is then available for the load itself.

2.2.5. Voltage limitation

The output voltage limitation is built around R106, R105, R108, C114 and the corresponding OPamp of the TSM 101.

R 106, R 105 create a bridge divider of the output voltage, in order to compare that fraction to the reference voltage of the TSM 101. The voltage limit is set by the formula:

$$V_{out} = V_{ref} \cdot \left(\frac{R105 + R106}{R105} \right)$$

If the voltage limit is reached, the cable AND of the TSM 101 allow the voltage limitation circuit to force the whole loop to reduce the output power.

The stability of the voltage limitation loop is done with R108 and C114.

For human body protection against electrical shocks, this limit has been set to around 40 V, as advise in safety standards.

2.3. No load operation

The design of the VIPer53 is intended to enter into burst mode when output see a low load. The application designer must avoid to enter in hiccup mode (or bad burst mode) when no load is connected.

The resistors R106 and R105 has been designed in the application in order to have the VIPer53 in burst mode when no load is connected. A sufficient current is drawn into R106 and R105, dissipating the few power transferred to the secondary side of the transformer during the burst mode, using the minimum turn-on time (see Figure 7, Figure 9 and Section 4.8, Figure 17 for measurements).

2.4. Short circuit operation

Due to current generator structure, there is no malfunction or damage when used in short circuit condition. The current is by definition limited. The output power is low in that condition (refer to Section 4.8 and Figure 18 for measurements).

2.5. Low Voltage Load

When using very low voltage load (less than 4 volts at output), some instability problem may appears, depending of the load type (inductive or capacitive load, etc.).

Poles and zeros vary too much, which lead to make instable the whole transfer function.

This instability may be associated with audible noise due to some low frequency oscillations. The user must avoid using loads which have a voltage below than 4V, in order to ensure a correct operation of the power supply.

3. Transformer design

3.1. Primary Inductance

The primary inductance has been set to 0.5mH, according to the output power required, and the (minimum specification of) current capability of the VIPer53.

The VIPer software helps to define the number of turns of the primary inductance. It provides a result of 52 turns, in 2 wires. A diameter of 0.4mm has been chosen.

3.2. Primary Auxiliary winding

The VIPer53 must be supplied with at least 12.8 V, for a correct operation. This winding is also used in forward mode. The turn ratio between primary winding and primary auxiliary winding according to the minimum input voltage (100 V_{DC}) is 0.18.

A value of 0.21 will be used with 11 turns on auxiliary. At maximum input voltage (400 V_{DC}), the auxiliary supply then will be 85 V. This will provide constraint on the voltage regulator for the VIPer53.

3.2.1. Secondary winding

The output voltage may vary from 4 V up to 40 V, and the reflected voltage must not exceed 100 V. The turn ratio should be 0.5 (26 turns) in order to avoid current mode instability.

A diameter of 0.7mm is provided by VIPer software.

3.3. Secondary Auxiliary winding

This secondary auxiliary output must guaranty a voltage from minimum 6 V up to maximum 32 V (supply voltage range of the TSM 101). The turn ratio is 0.077 (4 turns). This provide a supply voltage from 7.7V up to 30.8 V, which is in line with the specification of the TSM 101.

3.4. Summary of transformer

Table 2 summarise the specification of the power supply transformer.


4. Measurements

The measurements done on the application board has been performed at room temperature (27°C), using an open application board, in still air condition.

Static measurements have been performed using a programmable electronic load, used as a voltage generator (so called "static load").

In order to be as close as possible of the LEDs load, dynamic measurements have been done using a discrete voltage generator, as described in Figure 3 (so called "dynamic load"). This present a similar load as LEDs according to serial resistance and parasitic capacitance.

Figure 3. Discrete Voltage Load

 

4.1. Switching cycle

Figure 4 and Figure 5 show the drain voltage and drain current respectively in discontinuous mode and continuous mode, with a 40 Watts static load, and input voltage respectively at 400 V and 100 V.

Figure 7 and Figure 9 present Drain voltage, Drain current, V_{COMP} and V_{OUT} voltage in burst mode. The output (static) load is 4 Watts (40 Volts, 100 mA), and input voltage is respectively at 100 V and 400 V.

AN2067 - APPLICATION NOTE

Table 2. Transformer specification

Parameter	Prim. Induct. or Turn Ratio	Number of Turns	Number of Wires	Wire diam. (mm)	Max Current (A)
Primary inductance	L _{prim} : 0.5mH L _{leak} < 4μH (0.8%) Core: E25H	52	2	0.4	2.3
Primary auxiliary winding	0.211	11	1	~0.2	<0.1
Secondary winding	0.5	26	1	0.7	1
Secondary auxiliary winding	0.077	4	1	~0.2	<0.1

Figure 4. Discontinuous mode (40W/V_{IN}=400V)

 


Figure 6. Burst mode (P_{load}=4W; V_{IN}=100V)

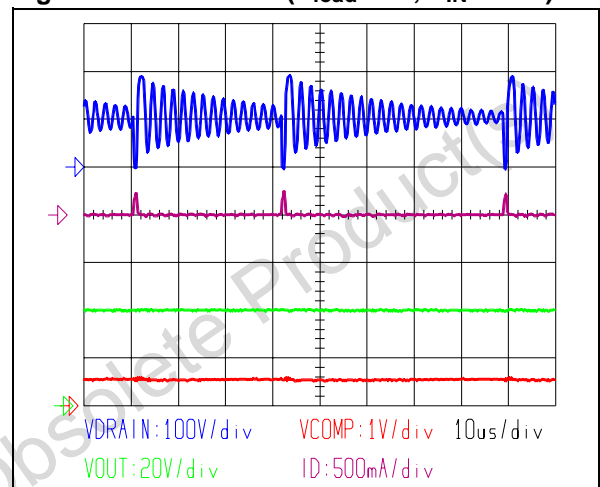


Figure 5. Continuous mode (40W/V_{IN}=100V)

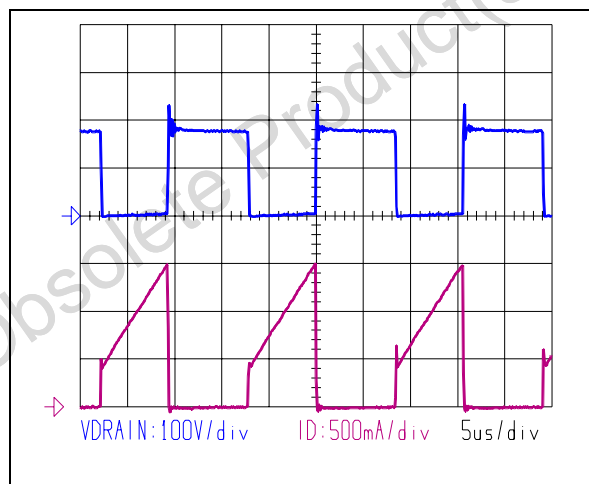


Figure 7. Burst mode (P_{load}=4W; V_{IN}=400V)


 


Figure 8. Dynamic response 50% duty cycle at 100Hz

 

4.2. Dynamic response

4.2.1. Discrete load

An external signal has been applied on connector J107 (node VREF_IN), in order to replace the static internal reference voltage of the TSM101 with a PWM signal.

The amplitude of this signal is 0 V (low level) - 1 V (high level) in order to get the full range 0 up to 1 A.

The frequency of this signal is around 100 Hz. The generator allow to adjust the duty cycle of this (PWM) signal from 10% up to 90%.

The load used during these measurements is a discrete load (dynamic load).

Figure 9. Dynamic response 10% duty cycle at 100Hz


 


Figure 8, Figure 9 and Figure 10 show the dynamic response of the current generator, when used in PWM mode, respectively with 50%, 10% and 90% of duty cycle.

10% and 90% of duty cycle at 100 Hz, is roughly the minimum and maximum duty cycle allowed to get an acceptable shape for the current pulse.

The minimum turn on/off time is around 1 ms. This provide a maximum frequency of 500 Hz (2 ms period).

Figure 10. Dynamic response 90% duty cycle at 100Hz

 

4.2.2. LEDs load

Figure 11 and Figure 12 represent the dynamic response on real load, respectively on 4 white LEDs, and 1 white LED.

The dynamic response is worst than using discrete load. It is also worst using 4 LEDs than using 1 LED. This typically shows the LED serial resistance limitation, as explain below in Section 2.2.4.

The poor dynamic response on LEDs load is because it has been optimized using the discrete load, which have different serial resistance.

There is a room for improvement on LEDs load, until the signal VCOMP still do not reach its maximum value (4.5V). Poles and zeros may be tune in order to improve the dynamic response of VCOMP, and then IOUT.

Figure 11. Dynamic response on 4 White LEDs


 



Figure 12. Dynamic response on 1 White LED

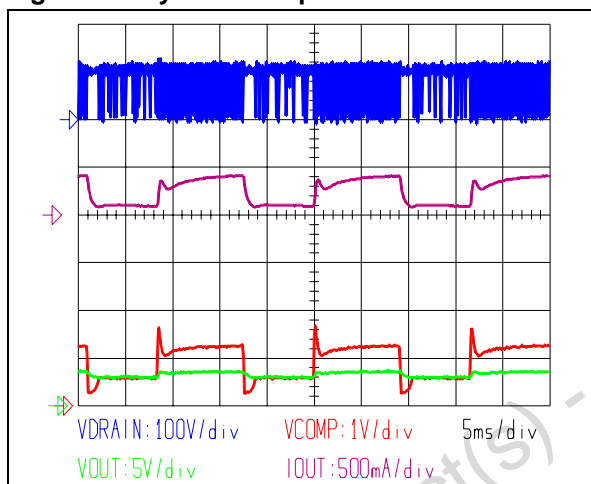

4.3. Line regulation

Figure 13 presents the output current variation versus AC line input voltage. It shows a variation of 0.4 %.


Figure 13. AC Line Regulation

 

4.4. Load regulation

The regulation versus the load is represented in Figure 14. The regulation is around 0.4 %.

Figure 14. Load Regulation

 


4.5. Voltage limitation

Figure 15 is the extension of the load regulation in Figure 14 (up to the voltage limit). Then, the voltage limitation act on the output power through the whole regulation loop, and the output current then decrease down to 0.

Note: Since the bridge divider has been slightly tune, the voltage limit may be different than these measures according to R105 and R106 standard values.

Figure 15. Voltage Limitation

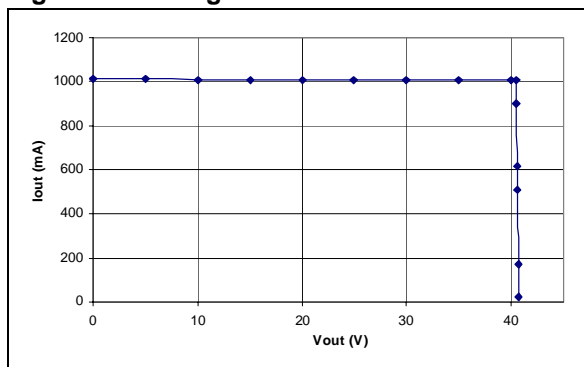

4.6. Power Supply Efficiency


Figure 16 shows the efficiency of the power supply when output power increases from 0 up to 40 Watts, using several input voltage. Output voltage vary while output current is 1 A.

The efficiency is lower than what could have been expect for an off line converter. This is mainly due



to the current generator structure of this application, which impose to have the supply of the VIPer53 connected on a forward winding, and because of its associated serial voltage regulator.

Figure 16. Efficiency ($I_{OUT}=1A$)

 

4.7. Efficiency Vs. output power ($V_{IN}=100V$)

Main contributors in the power budget are the transformer, the inrush current limiter, primary and secondary rectifier, and the clamber.

When output load increase, the ratio between the dissipated power of these main contributors and the output power decrease. This is because power of main contributors is quite constant versus the output load.

4.8. Extreme load conditions

Figure 17 and Figure 18 show the power supply consumption respectively when no load is connected at the output and in short circuit condition.

Figure 17. Input power in No Load mode

 


Figure 18. Input power in Short Circuit mode


 


Figure 19 presents Drain, COMP pin, Output voltage and Drain current during short circuit condition. Notice that the converter is in continuous mode ($V_{IN}=100V$).

Figure 19. Short circuit condition ($V_{IN}=100V$)

 

5. Board description

5.1. Printed Circuit Board

Figure 20 to Figure 22 present the PCB of the application. They respectively show all the layers of the PCB, the BOTTOM layer of the PCB, and then the TOP OVERLAY layer of the PCB.

Figure 20. All layers (not in scale)

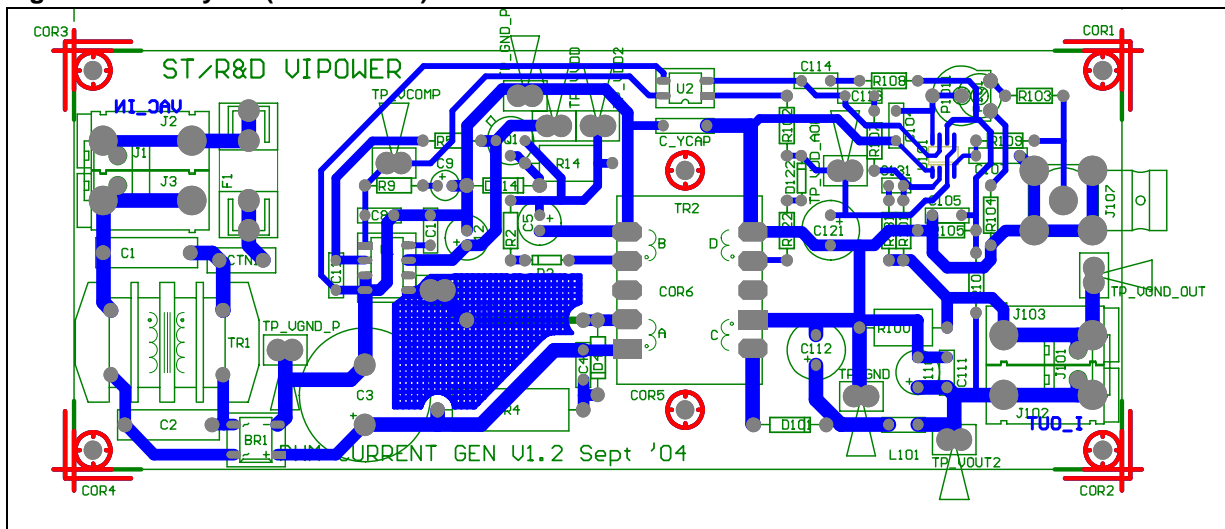


Figure 21. Bottom layer (not in scale)


 


Figure 22. Top Overlay layer (not in scale)

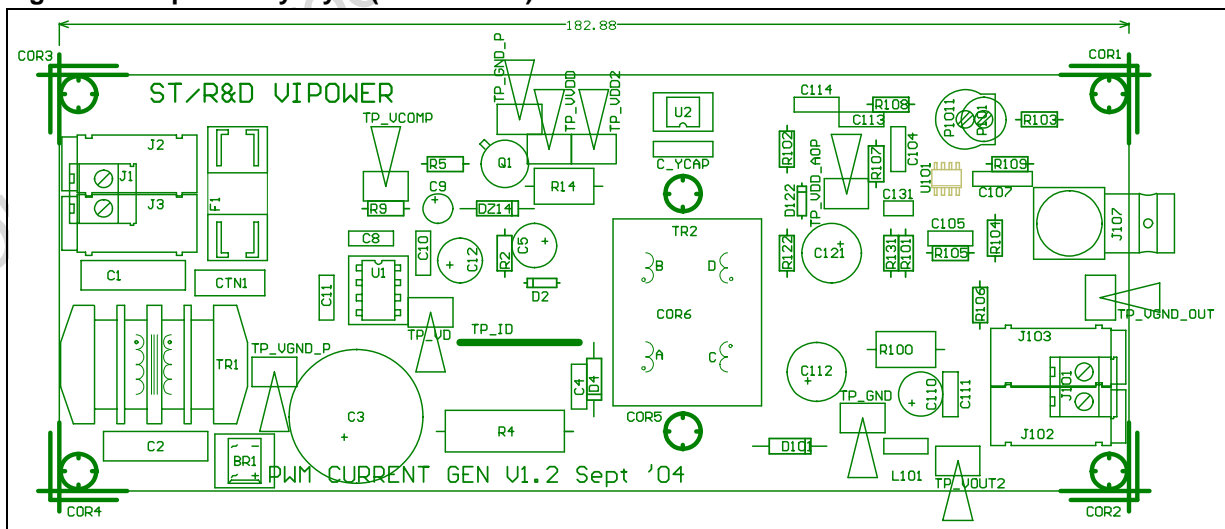

6. Bill of material

The Table 3 presents the bill of material of the application.

Table 3. Bill Of Material

Symbol	Description	Quantity
BR1	1A/500V	1
C1	100n/400V	1
C2	100n/400V	1
C3	100u/400V/159 PUL-SI	1
C4	1nF/250V	1
C5	1μF/100V/RLI135	1
C8	4.7nF	1
C9	470nF	1
C10	100nF	1
C11	4.7nF	1
C12	22μF/25V	1
C104	NC	1
C105	NC	1
C107	NC	1
C110	10uF/63V	1
C111	100nF	1
C112	220uF/63V/RLI 135	1
C113	22nF	1
C114	100nF	1
C121	22uF/40V	1
C131	10nF	1
COR1	CORNER	1
COR2	CORNER	1
COR3	CORNER	1
COR4	CORNER	1
COR5	CORNER	1
COR6	CORNER	1
CTN1		1
C_YCAP	2.2n/2KV	1
D2	BAS21	1
D4	EBR44-600	1
D101	STTH302	1
D122	BAS21	1
DZ14	12V/0.5W	1

AN2067 - APPLICATION NOTE

F1	FUSE	1
J1		1
J2		1
J3		1
J101		1
J102		1
J103		1
J107	Vref_in	1
L101	10uH	1
P101	1K	1
P1011	1K	1
Q1	BC546/VCEO=100V/1W	1
R2	10	1
R4	47K Ω /4W	1
R5	5.1K Ω	1
R9	6.8K Ω	1
R14	3.3K Ω /0.5W	1
R100	0.25 Ω	1
R101	12K Ω	1
R102	680 Ω	1
R103	2.2K Ω	1
R104	1 Ω	1
R105	1.8K Ω	1
R106	56K Ω	1
R107	6.8K Ω	1
R108	100K Ω	1
R109	1K Ω	1
R122	3.3 Ω	1
R131	1.8K Ω	1
TR1	LN_FILTER	1
TR2	E25	1
U1	STMicroelectronics VIPer53DIP	1
U2	PC817	1
U101	STMicroelectronics TSM101A	1

Information furnished is believed to be accurate and reliable. However, STMicroelectronics assumes no responsibility for the consequences of use of such information nor for any infringement of patents or other rights of third parties which may result from its use. No license is granted by implication or otherwise under any patent or patent rights of STMicroelectronics. Specifications mentioned in this publication are subject to change without notice. This publication supersedes and replaces all information previously supplied. STMicroelectronics products are not authorized for use as critical components in life support devices or systems without express written approval of STMicroelectronics.

The ST logo is a registered trademark of STMicroelectronics.
All other names are the property of their respective owners

© 2004 STMicroelectronics - All rights reserved

STMicroelectronics group of companies

Australia - Belgium - Brazil - Canada - China - Czech Republic - Finland - France - Germany - Hong Kong - India - Israel - Italy - Japan -
Malaysia - Malta - Morocco - Singapore - Spain - Sweden - Switzerland - United Kingdom - United States of America

www.st.com